

Circuits and Systems

Analysis vs Synthesis

Analysis problem:

Given the structure and the input of the system we determinate its output
--



The answer of analysis (systematic approach):

There is one answer

Synthesis problem:


Given the input and the output of the system we wish to find its structure




The answer of the synthesis (design approach):
--

Sometimes there is no answer and often the answer is not unique
--


The Available Elements for the Synthesis

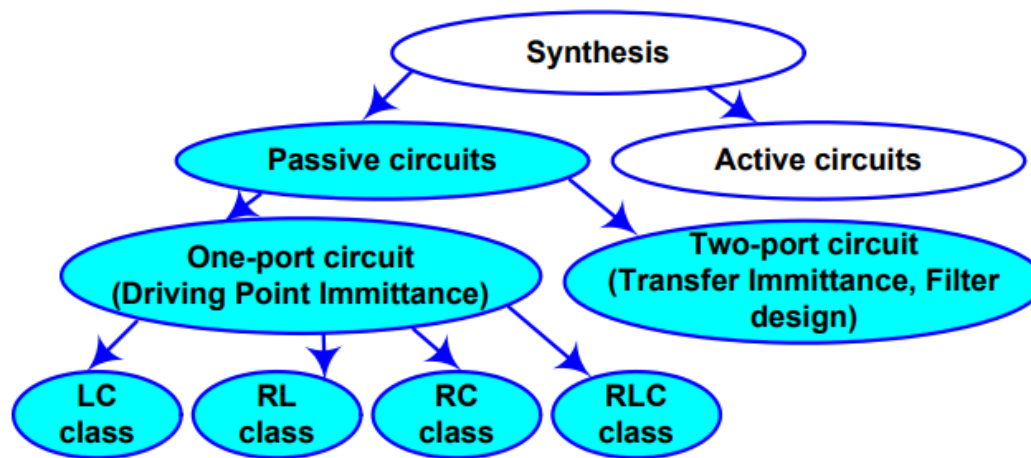

Synthesis of Passive Circuits

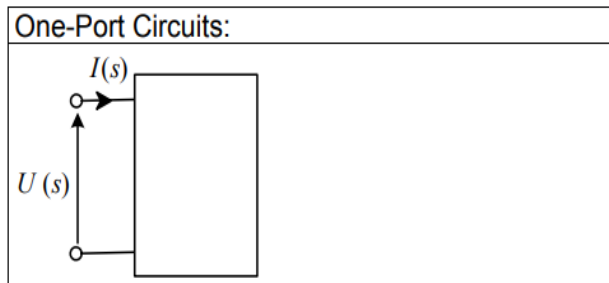

$\frac{U(s)}{I(s)}$	- driving point impedance
$\frac{I(s)}{U(s)}$	- driving point admittance

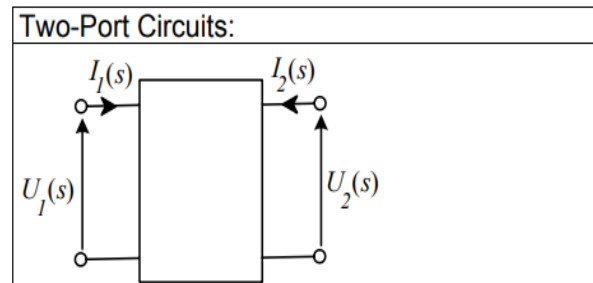

$\frac{U_1(s)}{I_1(s)}$	- driving point impedance
$\frac{I_1(s)}{U_1(s)}$	- driving point admittance
$\frac{U_2(s)}{I_1(s)}$	- transfer impedance
$\frac{I_2(s)}{U_1(s)}$	- transfer admittance

Additionally:

$\frac{U_2(s)}{U_1(s)}$	- voltage ratio
$\frac{I_2(s)}{I_1(s)}$	- current ratio

The only types of elements allowed are R, L and C (lumped or distributed). The constraints of stability and causality lead to mathematical conditions on the form of $Z(s)$ and $Y(s)$.

Immittance is the word used generically for impedances and admittances. In general, an immittance can be a driving point immittance or a transfer immittance.

Immittance and rational positive real function

A network with finite number of R,L,C elements has a driving point immittance, one-port impedance $Z(s)$ or admittance $Y(s)$, of the **rational** form:

$$F(s) = \frac{N(s)}{D(s)} = \frac{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}$$

Given function $F(s)$ can be **immittance** of design RLC passive circuit (in $Z(s)$ or $Y(s)$ form) only if fulfil requirements for being **rational positive real function**.

Condition for real character of $F(s)$ (necessary and sufficient):

C.R.1. coefficient of numerator $(a_n, a_{n-1}, \dots, a_1, a_0)$ and denominator $(b_m, b_{m-1}, \dots, b_1, b_0)$ polynomials must be real

Conditions for positive character of $F(s)$ (sufficient):

C.P.1. coefficient of numerator $(a_n, a_{n-1}, \dots, a_1, a_0)$ and denominator $(b_m, b_{m-1}, \dots, b_1, b_0)$ polynomials must have the same sign

C.P.2. power of "s" in numerator and denominator may differ at most by 1 $((n - m) \in \{-1, 0, 1\})$

C.P.3. Poles and zeros must lie on the left-hand half plane or on the imaginary axis

C.P.4. If the poles and zeros lie on the imaginary axis their must be single (real $s=0$ or in conjugate pairs $s = \pm j\omega$) and $F(s)$ must have positive, real residues for poles

($\text{res } F(s) = \lim_{s \rightarrow s_{pole}} (s - s_{pole}) \cdot F(s)$), and positive, real derivative for zeros $F'(s_{zero})$

C.P.5. replacing $s = j\omega$ obtained form must have positive real part $\text{Re}\{F(j\omega)\} \geq 0$ for $0 \leq \omega \leq \infty$

Examples

Verification process of $F(s)$ in point of possible realization as one-port RLC immittance (test of realizability)

Verified function ($F(s)$)	Check list of conditions		
$F(s) = \frac{s}{s^2 + 2s + 1}$ power of numerator $n=1$ zeros: $s=0$ power of denominator $m=2$ poles: $s_{1,2}=-1$	C.R.1	all coefficient real	O.K.
	C.P.1	all coefficient with the same sign	O.K.
	C.P.2.	power of "s" in numerator and denominator differs by 1 $n-m=-1$	O.K.
	C.P.3	all zeros and poles lie on the left-hand half plane or on the imaginary axis	O.K.
	C.P.4	only one zero lie on the imaginary axis and its real the derivative in $s=0$ is real and positive $F'(s=0) = \frac{(s^2 + 2s + 1) - 2s \cdot s}{(s^2 + 2s + 1)^2} \Big _{s=0} = 1$	O.K.

$F(s) = \frac{s}{s^2 + 2s + 1}$	C.P.5	$F(j\omega) = \frac{j\omega}{(j\omega)^2 + 2j\omega + 1} = \frac{j\omega}{1 - \omega^2 + 2j\omega} =$ $= \frac{j\omega \cdot [(1 - \omega^2) - j2\omega]}{(1 - \omega^2)^2 + 4\omega^2} = \frac{2\omega^2 + j\omega(1 - \omega^2)}{(1 - \omega^2)^2 + 4\omega^2};$ <p>Thus, $\text{Re}\{F(j\omega)\} = \frac{2\omega^2}{(1 - \omega^2)^2 + 4\omega^2}$ and its real and positive for all $0 \leq \omega \leq \infty$</p>	O.K.
Final decision: Circuit possible for design and realization in RLC passive class			

Verified function (F(s))	Check list of conditions		
$F(s) = \frac{s^2 - 1}{s^2 + 3s + 2}$ power of numerator n=2 zeros: $s_1=1, s_2=-1$ power of denominator m=2 poles: $s_1=-1, s_2=-2$	C.R.1	all coefficient real	O.K.
	C.P.1	there is one coefficient which sign differs from the others	NOT O.K.
	C.P.2.		
	C.P.3		
	C.P.4		
	C.P.5		
Final decision: Circuit can not be design and realize in RLC passive class			
Verified function (F(s))	Check list of conditions		
$F(s) = s + j$ power of numerator n=1 zeros: $s_1=-j$ power of denominator m=0	C.R.1	there is one complex coefficient	NOT O.K.
	C.P.1	all coefficient with the same sign	O.K.
	C.P.2.	power of "s" in numerator and denominator differs by 1 $n-m=1$	O.K.
	C.P.3	all zeros and poles lie on imaginary axis	O.K.
	C.P.4	there is zero $s=-j$ which lies on imaginary axis but hasn't got its conjugate pair $s=j$	NOT O.K.
	C.P.5		
Final decision: Circuit can not be design and realize in RLC passive class			

Foster Synthesis

First Foster Form

$$Z(s) = \frac{H(s^2 + \omega_1^2)(s^2 + \omega_3^2) \dots (s^2 + \omega_m^2)}{(s^2 + \omega_2^2)(s^2 + \omega_4^2) \dots (s^2 + \omega_r^2)}$$


where $0 \leq \omega_1^2 \leq \omega_2^2 \leq \omega_3^2 \leq \dots$

and $m = r \pm 1$

By partial fraction expansion we can write:

$$Z(s) = k_\infty s + \frac{k_0}{s} + \sum_{p=2,4,\dots}^r \frac{k_p s}{s^2 + \omega_p^2}, \quad k_\infty, k_0 \geq 0, k_p > 0$$

This corresponds to the following circuit realisation:

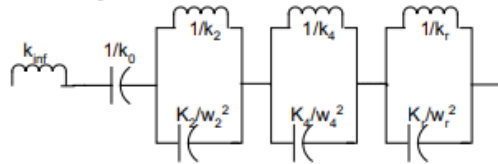

Example 1

We will consider the following simple driving point impedance function, where $\omega_1 > 0$ and $m = r - 1$:

$$Z(s) = \frac{s^2 + 1}{s(s^2 + 2)}$$


By partial fraction expansion we get:

$$Z(s) = \frac{A}{s} + \frac{Bs}{s^2 + 2} = \frac{A(s^2 + 2) + Bs^2}{s(s^2 + 2)}$$

$$\therefore A + B = 1, \quad 2A = 1$$

$$A = 1/2, B = 1/2$$


This corresponds to the circuit shown:

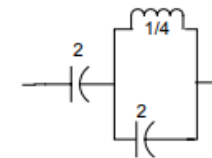

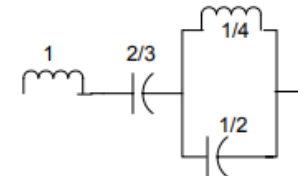Example 2

$\omega_1 > 0$ and $m = r + 1$:

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)} = s + \frac{3}{2s} + \frac{s}{2(s^2 + 2)}$$




Foster Synthesis

Second Foster Form

Example 1


$$Z(s) = \frac{s^2 + 1}{s(s^2 + 2)} \Rightarrow Y(s) = \frac{s(s^2 + 2)}{s^2 + 1} = s + \frac{s}{s^2 + 1}$$

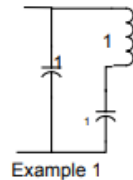

Example 1

Example 2

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)} \Rightarrow Y(s) = \frac{s(s^2 + 2)}{(s^2 + 1)(s^2 + 3)} = \frac{s}{2(s^2 + 1)} + \frac{s}{2(s^2 + 3)}$$

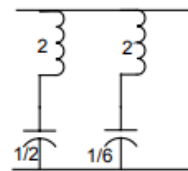

Example 2

Thank you for your attention.

